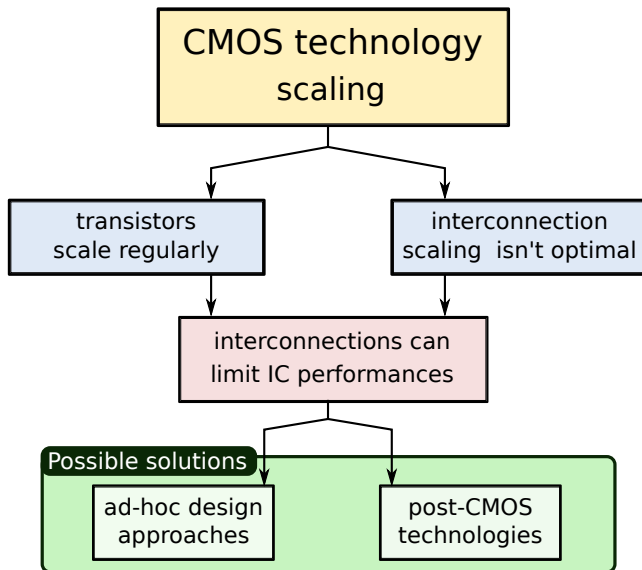


Logic synthesis techniques for switching nano-crossbar arrays

Anna Bernasconi, Valentina Ciriani, Luca Frontini, Valentino Liberali,
Gabriella Trucco, Tiziano Villa

Problem and proposed solutions




Interconnections in CMOS

Trend in Integrated Circuit industry:


- Improve throughput
- Reduce area
- Reduce power consumption

Technology scaling:

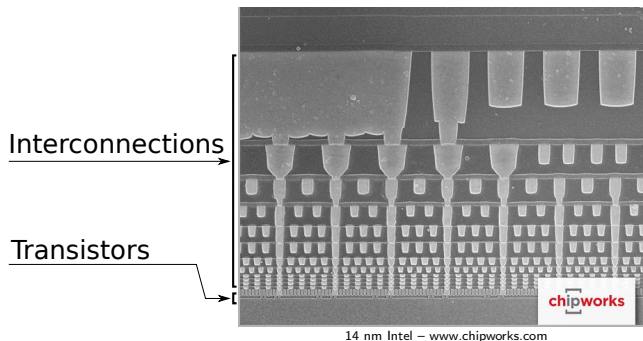- Exploits the vertical dimension
- The number of metal layer increases
- Interconnections scaling isn't optimal





New design approaches are needed

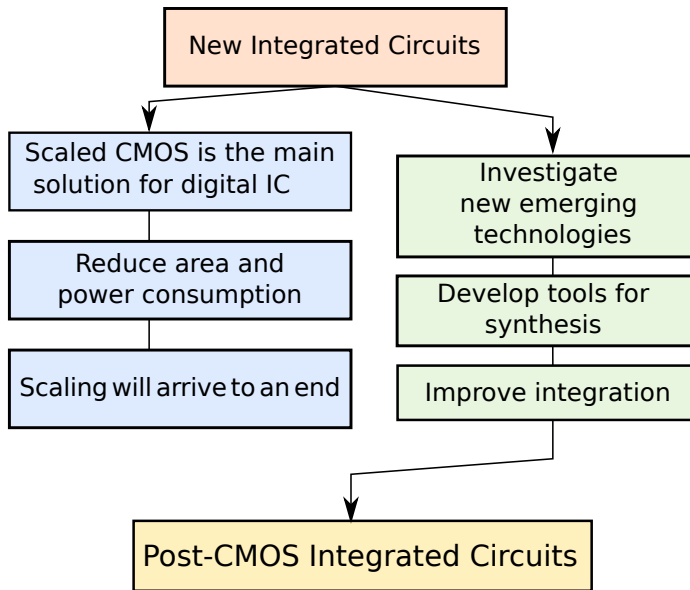

The Switching Lattices

Switching Lattices are **two-dimensional** array of **four-terminal** switches

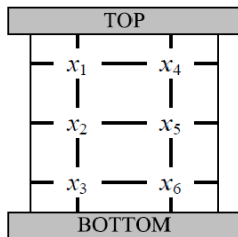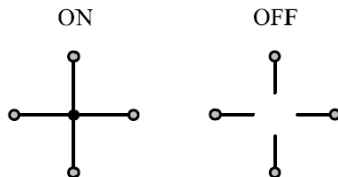- When switches are **ON** all terminals are connected, when **OFF** all terminals are disconnected
- Each switch is controlled by a boolean literal, **1** or **0**
- The boolean function f is the SOP of the literals along each path from **top** to **bottom**
- $f = x_1x_2x_3 + x_1x_2x_5x_6 + x_4x_5x_2x_3 + x_4x_5x_6$




Switching Lattices

Switching Lattices:


- are two dimensional array of four-terminal switches
- emerging post-CMOS technology

A lattice output is:

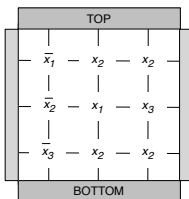
- 1 if there is a connection between top and bottom
 - 0 otherwise
 - Gray cells are ON
 - White cells are OFF
 - a), b): the 4-terminal switching network and the lattice describing
- $$f = \bar{x}_1\bar{x}_2\bar{x}_3 + x_1x_2 + x_2x_3$$
- c), d): the lattice with input (1,1,0) and (0,0,1)




(a)

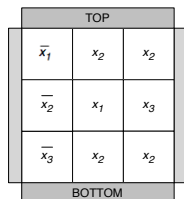

(b)

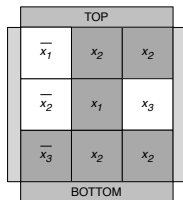

(c)

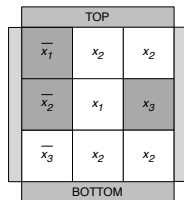


(d)

The synthesis methods


Altun-Riedel, 2012

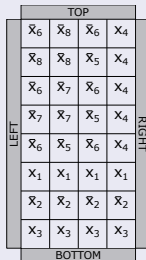- Synthesizes f and f^D from **top to bottom** and **left to right**
- It produces lattices with size growing **linearly** with the SOP
- Time **complexity is polynomial** in the number of products



Gange-Søndergaard-Stuckey, 2014

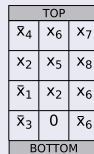- f is synthesized from **top to bottom**
- The synthesis problem is formulated as a **satisfiability problem**, then the problem is solved with a SAT solver
- The synthesis method searches for better implementations starting from an upper bound size
- The synthesis loses the possibility to generate both f and f^D




In both examples the synthesized function is:

$$f = \bar{x}_8\bar{x}_7\bar{x}_6x_3\bar{x}_2x_1 + \bar{x}_8\bar{x}_7\bar{x}_5x_3\bar{x}_2x_1 + x_4x_3\bar{x}_2x_1$$

Disjunction and conjunction of lattices


$f + g$

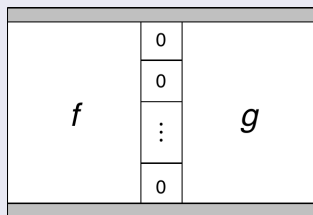- separate the paths from top to bottom for f and g
- add a column of 0s
- add padding rows of 1s if lattices have different number of rows




$f \cdot g$

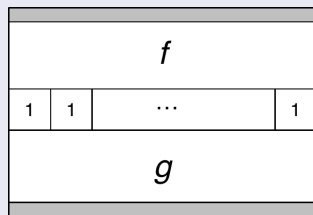- any top-bottom path of f is joined to any top-bottom path of g
- add a row of 1s
- add padding columns of 0s if lattices have different number of columns



Approach to the synthesis problem

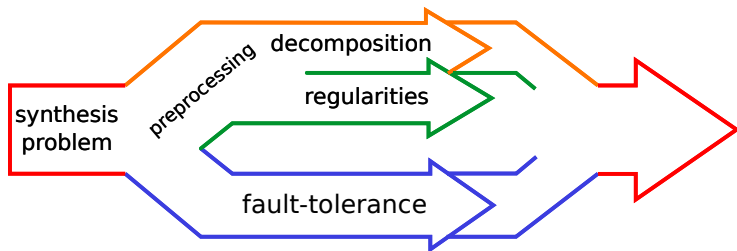

Different approaches can be used to optimize lattice synthesis.

Common goals are:

- Produce optimal-size lattices
- Reduce synthesis time
- Find efficient methods for sub-optimal lattice synthesis

Use sub-optimal lattices when optimal synthesis requires too much computing time or memory

Preprocessing: decomposition example

$$z4(2) = x_3\bar{x}_4\bar{x}_6\bar{x}_7 + x_1\bar{x}_3x_4\bar{x}_6 + \bar{x}_1x_3\bar{x}_6\bar{x}_7 + \bar{x}_3\bar{x}_4x_6\bar{x}_7 + x_1x_3x_4x_6 + x_1\bar{x}_3\bar{x}_6x_7 + \bar{x}_1x_3\bar{x}_4\bar{x}_6 + \bar{x}_3x_4\bar{x}_6x_7 + \bar{x}_1\bar{x}_3\bar{x}_4x_6 + x_1x_3x_6x_7 + x_3x_4x_6x_7$$

The lattice size is 12×12

P-circuit representation:

$$P(z) = \bar{x}_1 S(z^-) + x_1 S(z^\neq) + S(z^!)$$

$$S(z^-) = \bar{x}_3\bar{x}_4x_6 + x_3\bar{x}_4\bar{x}_6 + \bar{x}_3x_6\bar{x}_7 + x_3\bar{x}_6\bar{x}_7$$

$$S(z^\neq) = x_3x_4x_6 + \bar{x}_3x_4\bar{x}_6 + x_3x_6x_7 + \bar{x}_3\bar{x}_6x_7 + \bar{x}_3\bar{x}_4x_6\bar{x}_7 + x_3\bar{x}_4\bar{x}_6\bar{x}_7$$

$$S(z^!) = x_3x_4x_6x_7 + \bar{x}_3x_4\bar{x}_6x_7$$

	$x_6 x_7$			
$x_3 x_4$	00	01	11	10
00	0	0	1	1
01	0	1	0	1
11	1	0	1	0
10	1	1	0	0

$x_1 = 0$

	$x_6 x_7$			
$x_3 x_4$	00	01	11	10
00	0	1	0	1
01	1	1	0	0
11	0	0	1	1
10	1	0	1	0

$x_1 = 1$

	$x_6 x_7$			
$x_3 x_4$	00	01	11	10
00	0	0	1	1
01	0	0	0	1
11	1	0	0	0
10	1	1	0	0

z^-

	$x_6 x_7$			
$x_3 x_4$	00	01	11	10
00	0	1	0	1
01	1	1	0	0
11	0	0	1	1
10	1	0	1	0

z^\neq

	$x_6 x_7$			
$x_3 x_4$	00	01	11	10
00	0	0	0	0
01	0	1	0	0
11	0	0	1	0
10	0	0	0	0

$z^!$

\bar{x}_1	\bar{x}_1	\bar{x}_1	\bar{x}_1	0	x_1	x_1	x_1	x_1	x_1	x_1	0	x_4	x_4
x_6	x_3	x_6	x_3	0	x_6	\bar{x}_3	x_6	\bar{x}_3	\bar{x}_3	\bar{x}_4	0	x_7	x_7
\bar{x}_3	\bar{x}_6	\bar{x}_3	\bar{x}_6	0	x_3	\bar{x}_6	x_3	\bar{x}_6	\bar{x}_4	\bar{x}_4	0	x_6	\bar{x}_3
\bar{x}_4	\bar{x}_4	\bar{x}_7	\bar{x}_7	0	x_6	\bar{x}_3	x_6	\bar{x}_3	\bar{x}_3	\bar{x}_7	0	x_3	\bar{x}_6
1	1	1	1	0	x_3	\bar{x}_6	x_3	\bar{x}_6	\bar{x}_7	\bar{x}_7	0	1	1
1	1	1	1	0	x_3	x_4	x_3	x_7	x_6	x_3	0	1	1
1	1	1	1	0	x_4	x_4	x_7	x_7	\bar{x}_3	\bar{x}_6	0	1	1

D-Reducible function

is a function that can be decomposed as:

$$f = \chi_A \cdot f_A$$

- χ_A is the characteristic function of an affine space A
- f_A is the projection of f onto A

\bar{x}_4	\bar{x}_2	\bar{x}_2	\bar{x}_2	\bar{x}_2	\bar{x}_2
x_2	\bar{x}_5	\bar{x}_5	x_4	\bar{x}_5	\bar{x}_5
\bar{x}_3	\bar{x}_3	\bar{x}_3	x_4	\bar{x}_3	x_4
x_5	\bar{x}_2	\bar{x}_2	x_2	\bar{x}_2	\bar{x}_2
\bar{x}_4	\bar{x}_4	\bar{x}_4	x_3	\bar{x}_4	x_3
x_1	x_1	x_1	x_1	x_1	x_1
x_{11}	x_{11}	\bar{x}_7	\bar{x}_7	\bar{x}_7	\bar{x}_7
x_9	x_9	\bar{x}_7	\bar{x}_7	\bar{x}_7	\bar{x}_7
x_{10}	x_{10}	\bar{x}_7	\bar{x}_7	\bar{x}_7	\bar{x}_7
x_8	x_8	x_8	x_8	x_8	x_8

x_3	\bar{x}_3	0
x_4	\bar{x}_4	0
x_1	x_1	0
x_8	x_8	0
1	1	1
x_3	\bar{x}_5	\bar{x}_3
\bar{x}_2	\bar{x}_2	x_2
x_{10}	1	x_5
x_{11}	\bar{x}_7	\bar{x}_3
x_9	\bar{x}_7	\bar{x}_7

$$f = x_1 x_2 \bar{x}_3 \bar{x}_4 x_5 x_8 x_9 x_{10} x_{11} + x_2 \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 x_8 x_9 x_{10} x_{11} + x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 \bar{x}_7 x_8 + x_1 \bar{x}_2 x_3 x_4 \bar{x}_7 x_8 + x_1 \bar{x}_2 \bar{x}_3 \bar{x}_4 \bar{x}_5 \bar{x}_7 x_8 + x_1 \bar{x}_2 x_3 x_4 \bar{x}_7 x_8$$

$$f_A = \bar{x}_2 x_3 \bar{x}_7 + \bar{x}_2 \bar{x}_5 \bar{x}_7 + x_2 \bar{x}_3 x_5 \bar{x}_6 + \bar{x}_2 x_3 x_9 x_{10} x_{11} + x_2 \bar{x}_3 x_5 x_9 x_{10} x_{11}$$

$$\chi_A = x_1 x_8 (\overline{x_3 \oplus x_4})$$

P-circuits

- **smaller lattices:** at least 24% of area reduction in 33% of functions
- **affordable computing time,** in a lot of cases find a solution in less time than the optimum one

D-reducible functions


- **smaller lattices:** at least 24% of area reduction in 15% of functions
- **reduction of computing time** by 50% to find a solution than the optimum one

Example on regularities: autosymmetric boolean functions

Autosymmetric functions

- Let V be a vector subspace of $(\{0, 1\}^n, \oplus)$. The set $A = \alpha \oplus V$, $\alpha \in \{0, 1\}^n$, is an *affine space* over V with *translation point* α .
- $V = \alpha \oplus A$, with α any point in A .

x_1	$\overline{x_1}$	0	x_1	$\overline{x_1}$
$\overline{x_2}$	x_2	0	x_2	$\overline{x_2}$
1	1	0	1	1
x_3	$\overline{x_3}$	0	x_3	$\overline{x_3}$
x_4	$\overline{x_4}$	0	$\overline{x_4}$	x_4

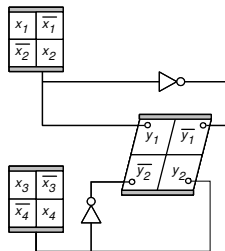

- $f(x_1, x_2, x_3, x_4) = x_1 \oplus x_2 \oplus x_3 \oplus x_4$.
- decomposing: $f = g(y_1, y_2) = y_1 \oplus y_2$, where $y_1 = x_1 \oplus x_2$ and $y_2 = x_3 \oplus x_4$
- Multi-lattice: the sum of the areas of the lattices is smaller than the area of the optimum single-lattice

Autosymmetric functions decomposition

- **smaller lattices:** at least 53% of area reduction in 48% of functions
- **affordable computing time:** in some cases is possible to find a solution in less time than the optimum one
- Some decomposed functions have **smaller total area** w.r.t. the lattice size in optimum case.

Drawbacks:

- Routing complexity increases
- It is necessary to add some inverters

Switching Lattices and Defect Tolerance

- The switching lattices are made of self assembled systems
- The probability to have a defect on a single cell is up to 10%

- We consider stuck-at-one and stuck-at-zero fault
- Different synthesis methods produce lattices with different sensitivity to faults
- Current work aims at **developing a synthesis method that can improve defect tolerance**

Given Logic Function

$$f = x_4 \bar{x}_5 x_7 + \bar{x}_4 x_6 \bar{x}_7 + \bar{x}_4 x_5 \bar{x}_6 x_7 + x_4 \bar{x}_6 \bar{x}_7 + x_4 x_6 x_7$$

x_4	\bar{x}_7	x_5	x_4, \bar{x}_7	x_4
\bar{x}_5	$x_6, \bar{x}_4, \bar{x}_7$	\bar{x}_4	\bar{x}_7	x_6
x_7	\bar{x}_4	$x_7, \bar{x}_4, \bar{x}_6$	\bar{x}_6	x_7
x_4	\bar{x}_7	\bar{x}_6	$x_4, \bar{x}_6, \bar{x}_7$	x_4
x_4, x_7	x_6	x_7	x_4	x_4, x_6, x_7

Possible Literal Appointments

a)

x_4	\bar{x}_7	x_5	x_4	x_4
\bar{x}_5	\bar{x}_7	\bar{x}_4	\bar{x}_7	x_6
x_7	\bar{x}_4	x_7	\bar{x}_6	x_7
x_4	\bar{x}_7	\bar{x}_6	\bar{x}_7	x_4
x_4	x_6	x_7	x_4	x_7

b)

\bar{x}_7	x_4	\bar{x}_7	x_5	x_4	x_4
\bar{x}_7	\bar{x}_5	\bar{x}_7	\bar{x}_4	\bar{x}_7	x_6
\bar{x}_4	x_7	\bar{x}_4	x_7	\bar{x}_6	x_7
\bar{x}_7	x_4	\bar{x}_7	\bar{x}_6	x_4	x_4
x_6	x_4	x_6	x_7	x_4	x_7

c)

- Using **Boolean function preprocessing** we found some techniques to **reduce synthesis time and area occupation** of switching lattices:
 - In many cases decomposition leads to smaller lattices w.r.t. sub-optimal Altun synthesis solution
 - Preprocessing can reduce computing time generating sub-optimal lattices
 - In the case of autosymmetric functions the sum of the areas of the synthesized lattices can be smaller than the area of the optimal single-lattice solution
- We found some preliminary techniques to reduce lattice sensitivity to faults
- In future we will work on lattice defectivity analysis and reduction of lattice sensitivity to faults

Thank you!